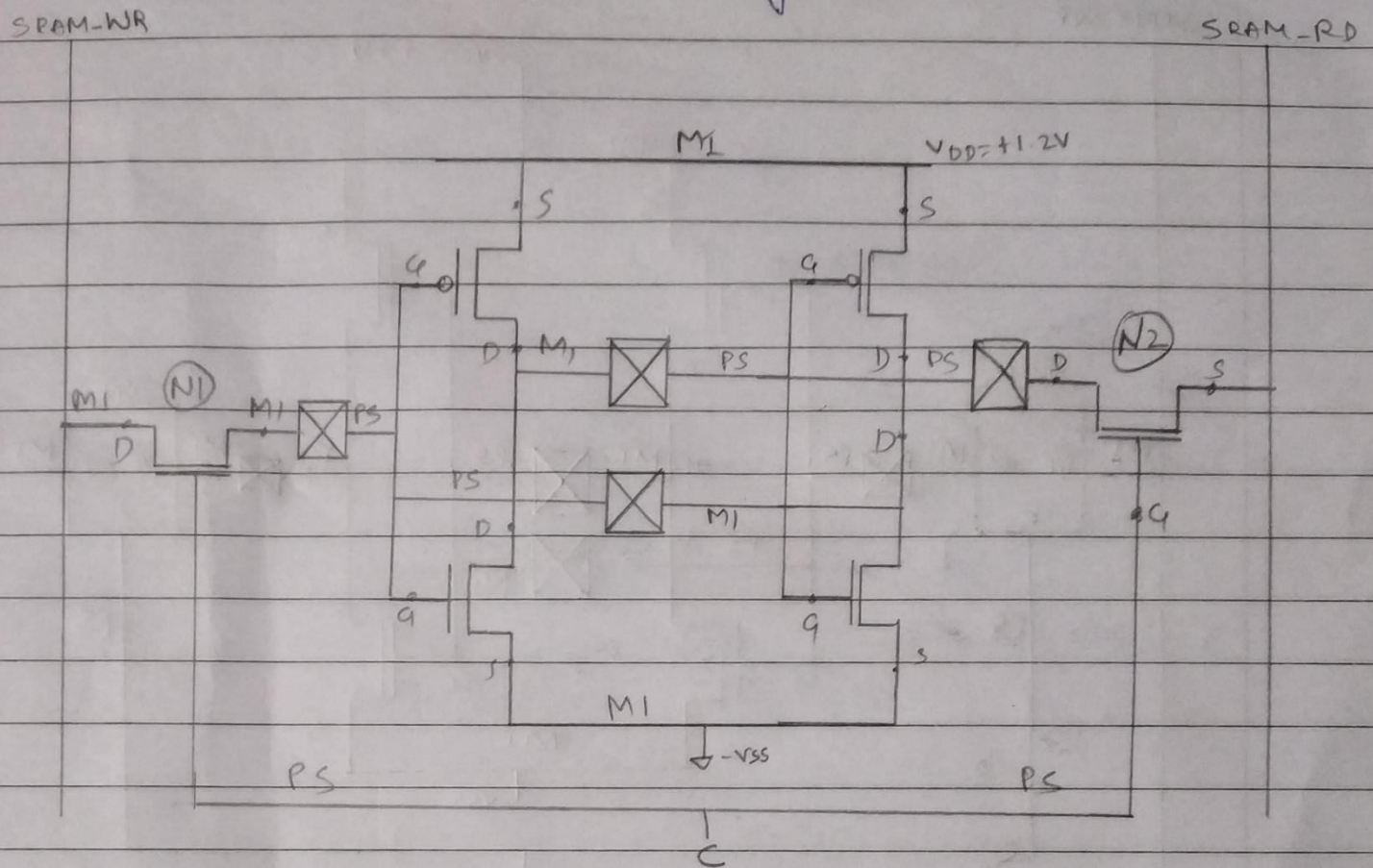


Class	:	BE - 8
Roll. No	:	42410
Assignment No.	:	B.3 (a,b)
Assignment Name	:	1 Bit SRAM Cell using NMOS and TG S/W
Date of Performance	:	30-11-2020

### ⊕ Assignment 3 : 1-bit SRAM cell

(3-a) :- 1-bit SRAM cell using NMOS switches!




⊕ N<sub>1</sub>, N<sub>2</sub> : NMOS s/w's

⊕ function Table:

C	SRAM-WR	SRAM-RD	Function
1	0	WEAK 1	
1	1	STRONG 0	
0	x	D/Hold	

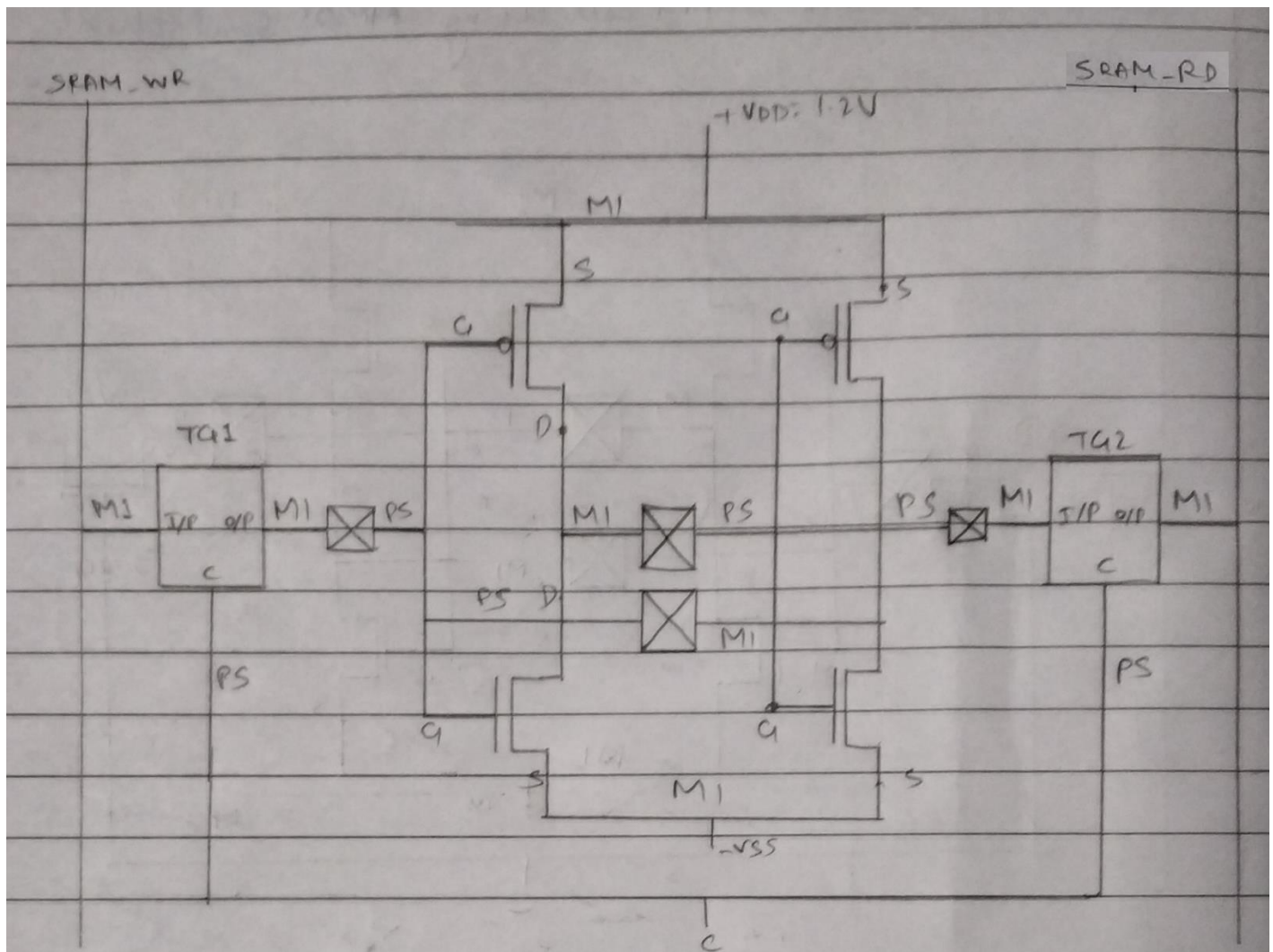(3-b) 1-bit SRAM cell using TC switches :-




⊗ TG1, TG2 : TG S/W's

⊗ Function - Table


C	SRAM_WR	SRAM_RD
1	0	STRONG - 1
1	1	STRONG - 0
0	X	0/HOLD

## LAYOUT

### 1) 1-bit SRAM using NMOS Switches

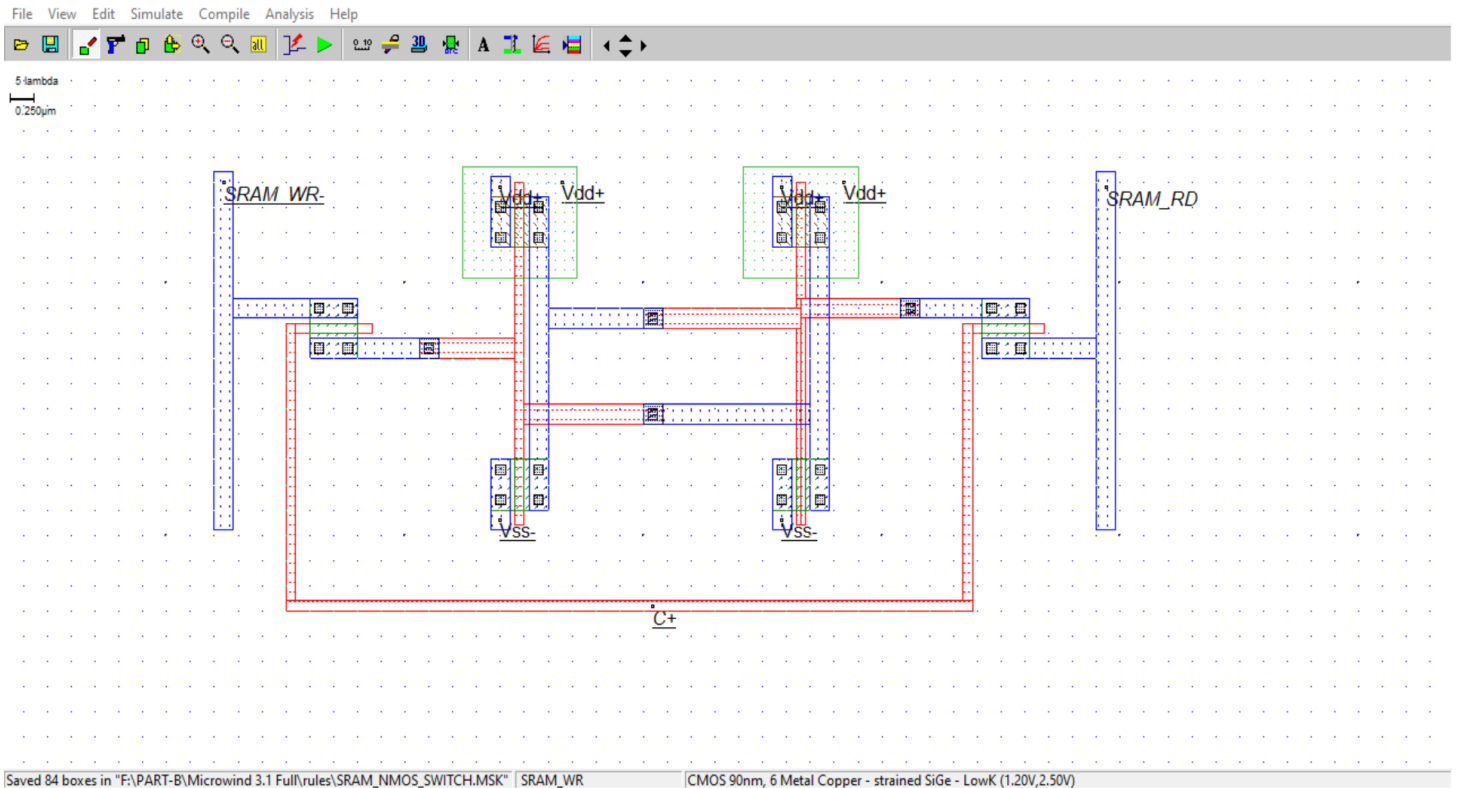


## 2) 1-bit SRAM cell using TG.

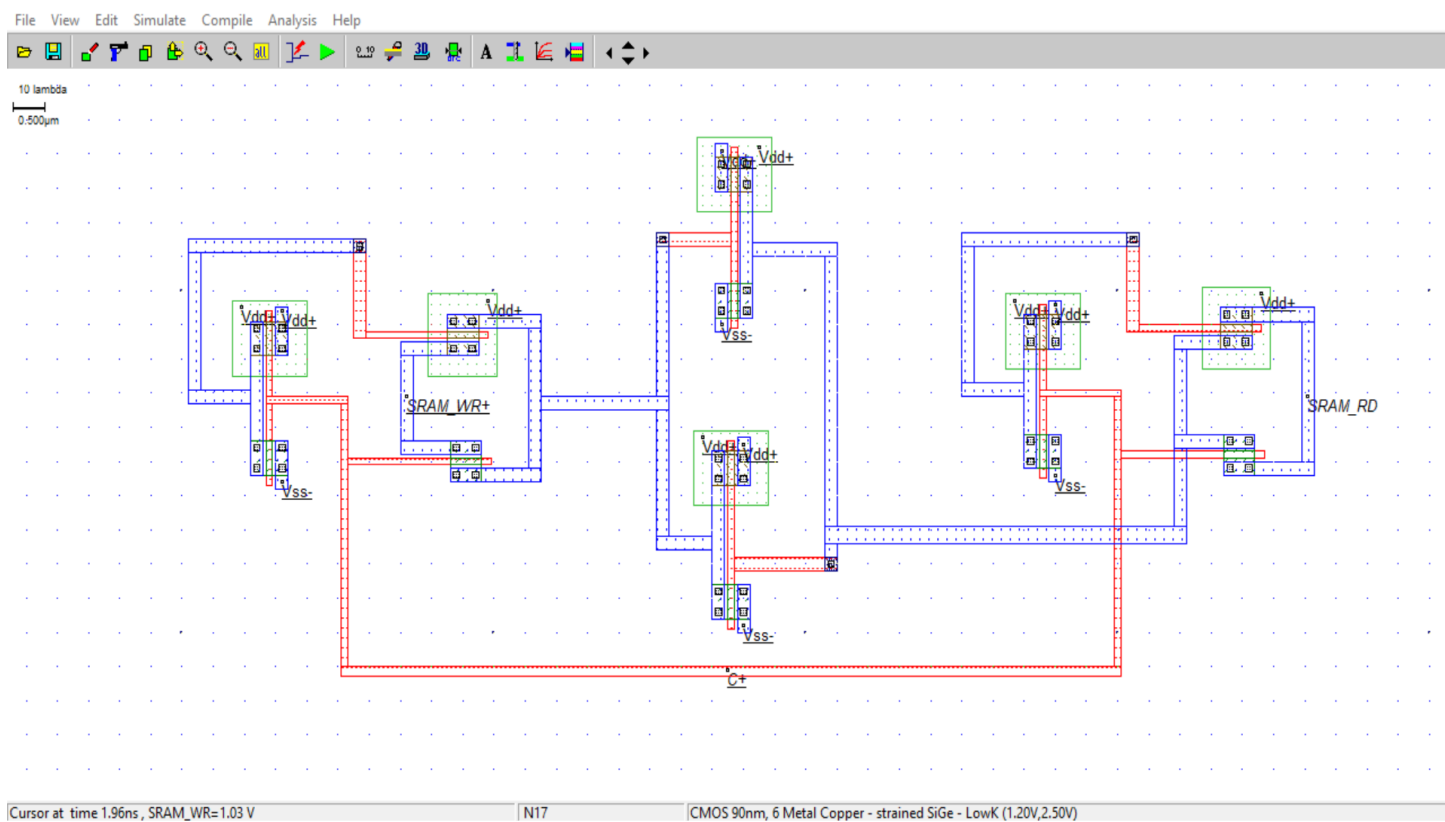


## WAVEFORMS

 
### 1. $C = 1$ , $\text{SRAM\_WRITE} = 0$ using NMOS Switches.


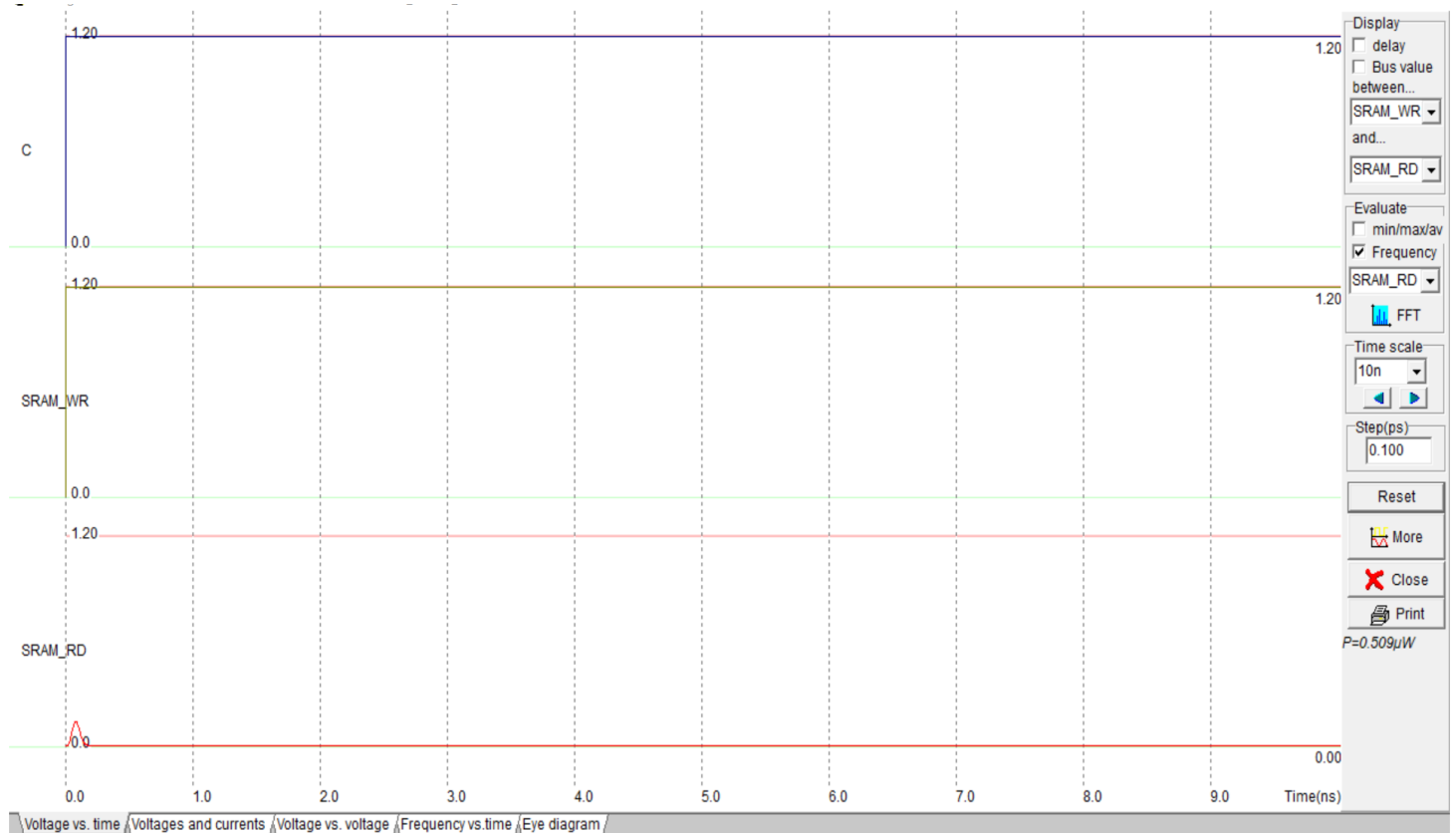
## 2. C =1, SRAM\_WRITE=1 using NMOS Switches.




### 3. C = 0 using NMOS Switches.

 




 
#### 4. C =1, SRAM\_WRITE=0 using TG Logic.


 
### 5. C =1, SRAM\_WRITE=1 using TG Logic.



## 6. C =0 using TG Logic.

 

## Conclusions:

Thus, we have:

- 1) Drawn the LAYOUT for 1-bit SRAM Cell using NMOS Switches and TG Switches using 90 nm Foundry.
- 2) Verified the waveforms of SRAM Cell.
- 3) Compared them with Truth table.
- 4) Verified the functionality of SRAM Cell.

