 


Class	:	BE - 8
Roll No	:	42410
Assignment No	:	3
Assignment Name	:	FIFO
Date of Performance	:	3-10 to 10-10

BLOCK DIAGRAM:




Function Table:


rst	CLK	wr.en	addr	data-out	full	Empty
1	x	x	x	$(00)_{16}$	0	1
0	\downarrow	1	$(00)_2$	NA	$0 \rightarrow 1$	0
0	\downarrow	0	$(11)_2$	data-in	0	0

MAIN VHDL PROGRAM:


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
use IEEE.NUMERIC_STD.ALL;
entity FIFO is
  Port
  (
    data_in : in  STD_LOGIC_VECTOR (7 downto 0);
    rst : in  STD_LOGIC;
    clk : in  STD_LOGIC;
    wr_en : in  STD_LOGIC;
    addr : in  STD_LOGIC_VECTOR (1 downto 0);
    data_out : out STD_LOGIC_VECTOR (7 downto 0);
    empty : inout STD_LOGIC;
    full : inout STD_LOGIC);
end FIFO;
architecture FIFO_ARCH of FIFO is
  TYPE MEMORY IS ARRAY(0 TO 3) OF STD_LOGIC_VECTOR(7 DOWNT0 0);
  SIGNAL MEM : MEMORY:=(X"00",X"00",X"00",X"00");
  CONSTANT all_zeros : MEMORY :=(others => (others=>'0'));
begin
  PROCESS(data_in,rst,clk,wr_en,addr,empty,full)
  BEGIN
    IF rst='1' THEN
      data_out<=X"00";
      MEM<=(X"00",X"00",X"00",X"00");
      empty<='1';
      full<='0';
    ELSIF FALLING_EDGE(clk) THEN
      IF (MEM(0)/=X"00") AND (MEM(1)=X"00") AND (MEM(2)/=X"00") AND (MEM(3)/=X"00") THEN
        empty<='0';
        full<='1';
      ELSE
        empty<='0';
        full<='0';
      END IF;
      IF wr_en='1' THEN  --WRITE
        CASE addr IS
          WHEN "00" => MEM(0)<=data_in;
          WHEN "01" => MEM(1)<=data_in;
          WHEN "10" => MEM(2)<=data_in;
          WHEN OTHERS => MEM(3)<=data_in;
        END CASE;
      ELSE  --READ
        CASE addr IS
          WHEN "00" => data_out<=MEM(0);-- MEM(0)<=X"00";
          WHEN "01" => data_out<=MEM(1);-- MEM(1)<=X"00";
          WHEN "10" => data_out<=MEM(2);-- MEM(2)<=X"00";
          WHEN OTHERS => data_out<=MEM(3);-- MEM(3)<=X"00";
        END CASE;
      END IF;
    END IF;
  END PROCESS;
end FIFO_ARCH;
```

RTL SCHEMATIC

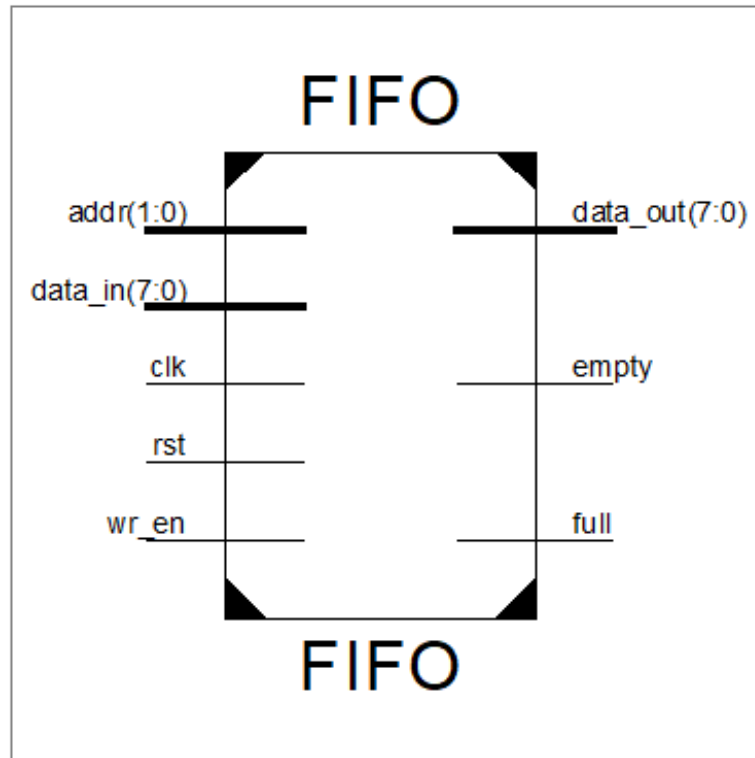


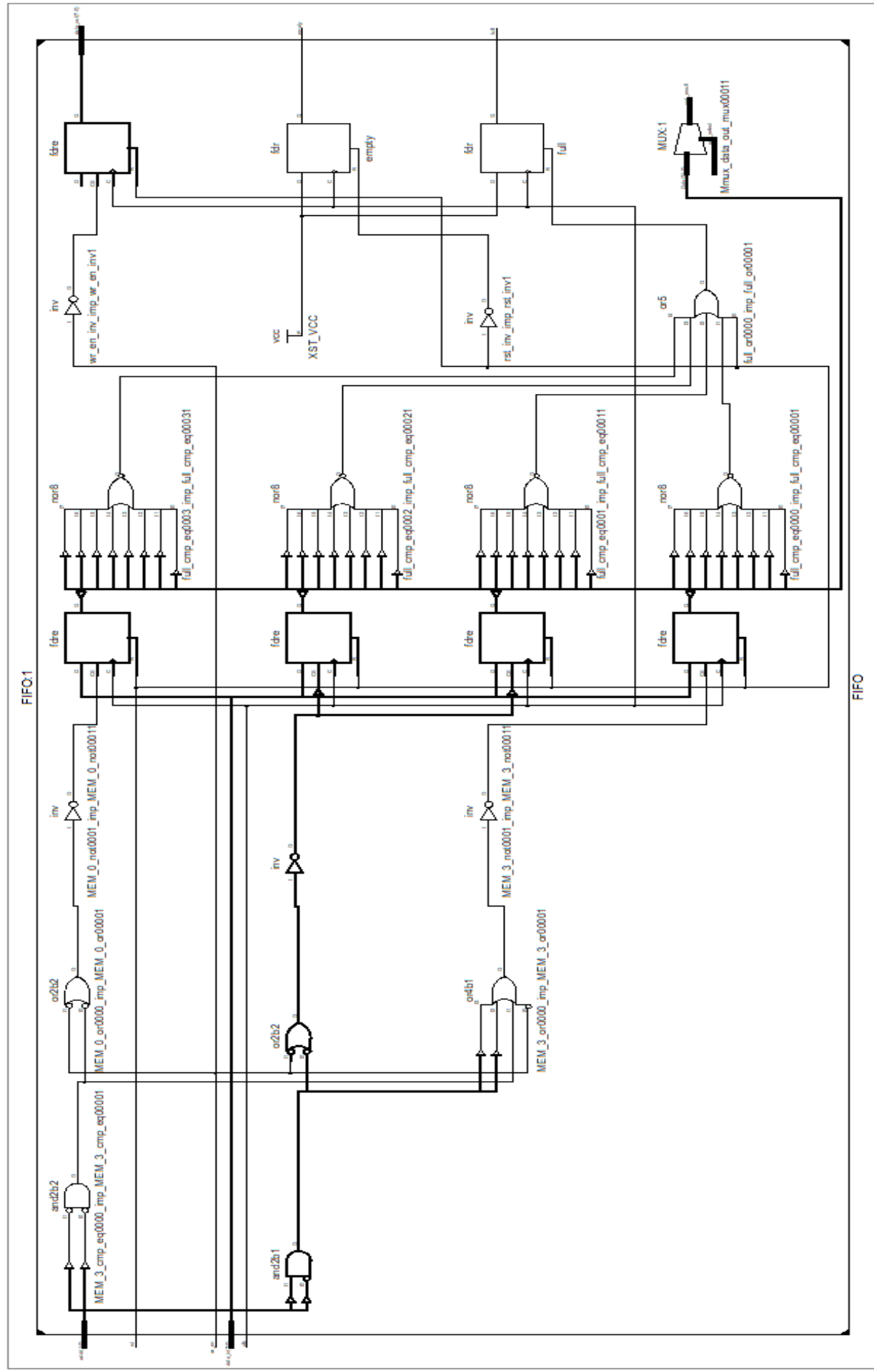

TECHNOLOGY SCHEMATIC

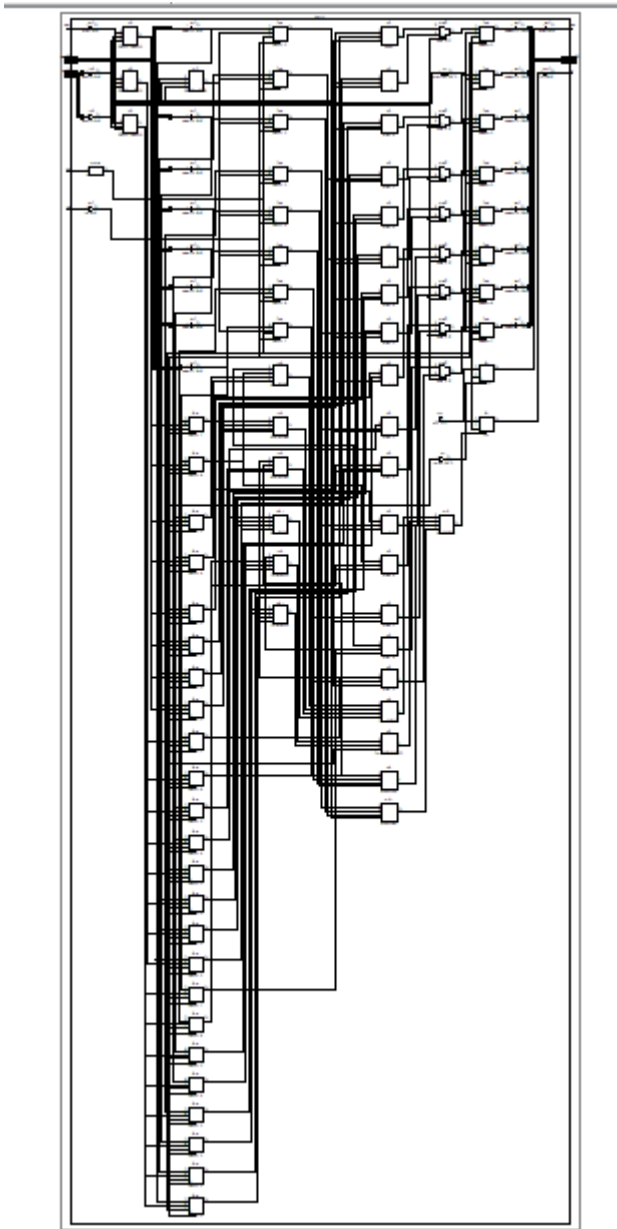

FIFO:1

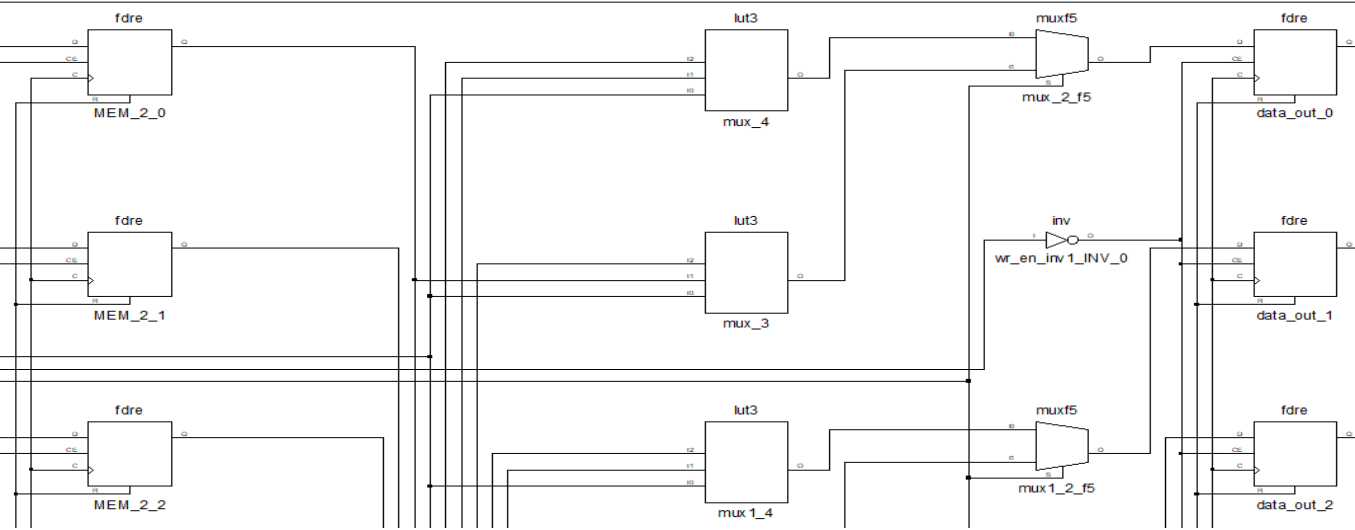

SYNTHESIS REPORT:

A) Device Utilisation Summary

=====

* Final Report *

=====

Final Results

RTL Top Level Output File Name : FIFO.ngr

Top Level Output File Name : FIFO

Output Format : NGC

Optimization Goal : Speed

Keep Hierarchy : No

Design Statistics

IOs : 23

Cell Usage :

BELS : 41

GND : 1

INV : 1

LUT2 : 1

LUT3 : 20

LUT4 : 8

LUT4_L : 2

MUXF5 : 8

FlipFlops/Latches : 42

FDC_1 : 1

FDCE_1 : 40

FDP_1 : 1

Clock Buffers : 1

BUFGP : 1

IO Buffers : 22

IBUF : 12

OBUF : 10

=====

Device utilization summary:

Selected Device : 3s250epq208-5

Number of Slices: 29 out of 2448 1%

Number of Slice Flip Flops: 41 out of 4896 0%

Number of 4 input LUTs: 32 out of 4896 0%

Number of IOs: 23

Number of bonded IOBs: 23 out of 158 14%

IOB Flip Flops: 1

Number of GCLKs: 1 out of 24 4%

Partition Resource Summary:

No Partitions were found in this design.

B) TIMMING REPORT

=====

TIMING REPORT

NOTE: THESE TIMING NUMBERS ARE ONLY A SYNTHESIS ESTIMATE.
FOR ACCURATE TIMING INFORMATION PLEASE REFER TO THE TRACE REPORT
GENERATED AFTER PLACE-and-ROUTE.

Clock Information:

-----+-----+-----+			
Clock Signal		Clock buffer(FF name)	Load
-----+-----+-----+			
clk		BUFGP	42
-----+-----+-----+			

Asynchronous Control Signals Information:

-----+-----+-----+			
Control Signal		Buffer(FF name)	Load
-----+-----+-----+			
rst		IBUF	42
-----+-----+-----+			

Timing Summary:

Speed Grade: -5

Minimum period: 4.085ns (Maximum Frequency: 244.801MHz)

Minimum input arrival time before clock: 3.933ns

Maximum output required time after clock: 4.040ns

Maximum combinational path delay: No path found

Timing Detail:

All values displayed in nanoseconds (ns)

TEST BENCH PROGRAM

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
use IEEE.NUMERIC_STD.ALL;

ENTITY FIFO_tb IS
END FIFO_tb;

ARCHITECTURE behavior OF FIFO_tb IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT FIFO
    PORT(
        data_in : IN std_logic_vector(7 downto 0);
        rst : IN std_logic;
        clk : IN std_logic;
        wr_en : IN std_logic;
            addr : in STD_LOGIC_VECTOR (1 downto 0);
        data_out : OUT std_logic_vector(7 downto 0);
        empty : INOUT std_logic;
        full : INOUT std_logic
    );
    END COMPONENT;

    --Inputs
    signal data_in : std_logic_vector(7 downto 0) := X"FF";
    signal rst : std_logic := '1';
    signal clk : std_logic := '0';
    signal wr_en : std_logic := '0';
        signal addr : STD_LOGIC_VECTOR (1 downto 0):="00";

    --BiDirs
    signal empty : std_logic;
    signal full : std_logic;

    --Outputs
    signal data_out : std_logic_vector(7 downto 0);

    -- Clock period definitions
    constant clk_period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: FIFO PORT MAP (
        data_in => data_in,
        rst => rst,
        clk => clk,
        wr_en => wr_en,
            addr => addr,
        data_out => data_out,
        empty => empty,
```

```

    full => full
  );

-- Clock process definitions
clk_process :process
begin
    clk <= '0';
    wait for clk_period/2;
    clk <= '1';
    wait for clk_period/2;
end process;

-- Stimulus process
stim_procDIN: process
begin
    data_in<= data_in +1;
    wait for 10 ns;
end process;


    stim_procRST: process
begin
    rst<= '1';
    wait for 40 ns;
    rst<= '0';
    wait for 160 ns;
end process;

    stim_procWREN: process
begin
    wait for 40 ns;
    wr_en<=NOT(wr_en);
end process;

    stim_procADDR: process
begin
    wait for 10 ns;
    addr<= addr+1;
end process;
END;

```

ISIM WAVEFORMS

 

PIN LOCKING REPORT

PlanAhead Generated physical constraints

```
NET "data_in[7]" LOC = P165;    #sw4-0
NET "data_in[6]" LOC = P167;    #sw4-1
NET "data_in[5]" LOC = P163;    #sw4-2
NET "data_in[4]" LOC = P164;
NET "data_in[3]" LOC = P161;
NET "data_in[2]" LOC = P162;
NET "data_in[1]" LOC = P160;
NET "data_in[0]" LOC = P153;    #sw4-7
NET "data_out[7]" LOC = P179;    #sw3-0
NET "data_out[6]" LOC = P180;    #sw3-1
NET "data_out[5]" LOC = P177;
NET "data_out[4]" LOC = P178;
NET "data_out[3]" LOC = P152;
NET "data_out[2]" LOC = P168;
NET "data_out[1]" LOC = P171;
NET "data_out[0]" LOC = P172;    #sw3-7
NET "clk" LOC = P132;
NET "reset" LOC = P204;         #k0
NET "enr" LOC = P184;          #sw2-6
NET "enw" LOC = P194;          #sw2-7
NET "fifo_empty" LOC = P199;#sw1-6
NET "fifo_full" LOC = P196;    #sw1-7
```

Conclusion:

Thus, we have:

- 1) Modeled a 4-bit ALU using Behavioral Modeling Style.
- 2) Observed following Schematics: **RTL & Technology Schematics** generated **Post-Synthesis**.
- 3) Interpreted **Device utilization Summary** in terms of LUTs, SLICES, IOBs, Multiplexers & D FFs used out of the available device resources.
- 4) Interpreted the TIMING Report in terms of Maximum combinational delay as indicative of the Maximum Operating Frequency.
- 5) Written a TESTBENCH to verify the functionality of 4-bit ALU & verified the functionality as per the TRUTH-TABLE, by observing ISIM Waveforms.
- 6) Used Plan Ahead Editor for pin-locking.
- 7) Prototyped the FPGA **XC3S250EPQ208-5** to realize 4-bit ALU & verified its operation by giving suitable input combinations