 


TITLE PAGE

Class	:	BE - 8
Roll. No	:	42428
Assignment No.	:	A. 1
Assignment Name	:	4-bit ALU
Date Of Performance	:	5-9-2020 to 19-9-2020

Block Diagram:



Truth-Table : A = 1010 B = 1100

F	Y	Y _{exp}	CARRY_SIGN
000	A . B	1000	0
001	$\overline{A \cdot B}$	0111	0
010	A + B	1110	0
011	$\overline{A + B}$	0001	0
100	$A \oplus B$	0110	0
101	$\overline{A \oplus B}$	1001	0
110	A add B	0110	1
111	A - B	0010	1

MAIN VHDL PROGRAM

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
use IEEE.NUMERIC_STD.ALL;




entity alu_4_1 is
    Port (
        A : in  STD_LOGIC_VECTOR (3 downto 0);
        B : in  STD_LOGIC_VECTOR (3 downto 0);
        F : in  STD_LOGIC_VECTOR (2 downto 0);
        Y : out STD_LOGIC_VECTOR (3 downto 0);
        CARRY_SIGN : out STD_LOGIC
    );
end alu_4_1;

architecture alu_4_1_arch of alu_4_1 is
    signal result: STD_LOGIC_VECTOR(4 DOWNTO 0):="00000";
begin
    process(A,B,F)
    begin
        case F is
            when "000" =>
                result<= '0' & (A AND B);
            when "001" =>
                result<= '0' & (A NAND B);
            when "010" =>
                result<= '0' & (A OR B);
            when "011" =>
                result<= '0' & (A NOR B);
            when "100" =>
                result<= '0' & (A XOR B);
            when "101" =>
                result<= '0' & (A XNOR B);
            when "110" =>
                result<= ('0' & A)+('0' & B);
            when others =>
                IF A < B THEN
                    result<= (NOT(('0' & A) + ('0' & (NOT B)) + 1))+1;
                ELSE
                    result <= ('0' & A)-('0' & B);
                END IF;
            end case;



        end process;

        Y <= result(3 downto 0);
        CARRY_SIGN <= result(4);
    end alu_4_1_arch;
```


RTL SCHEMATIC

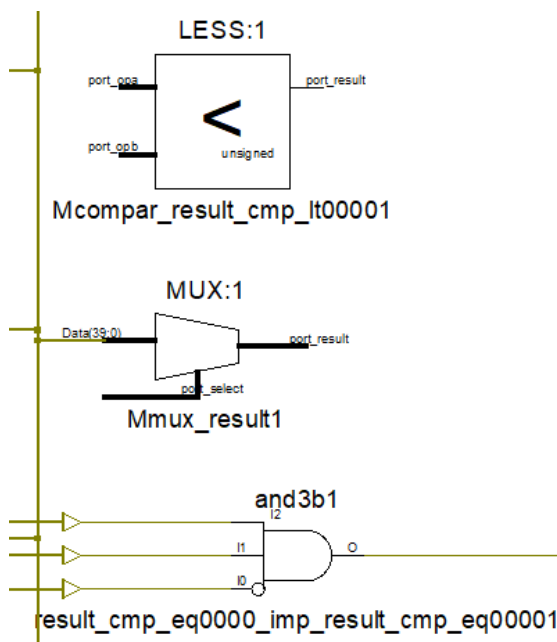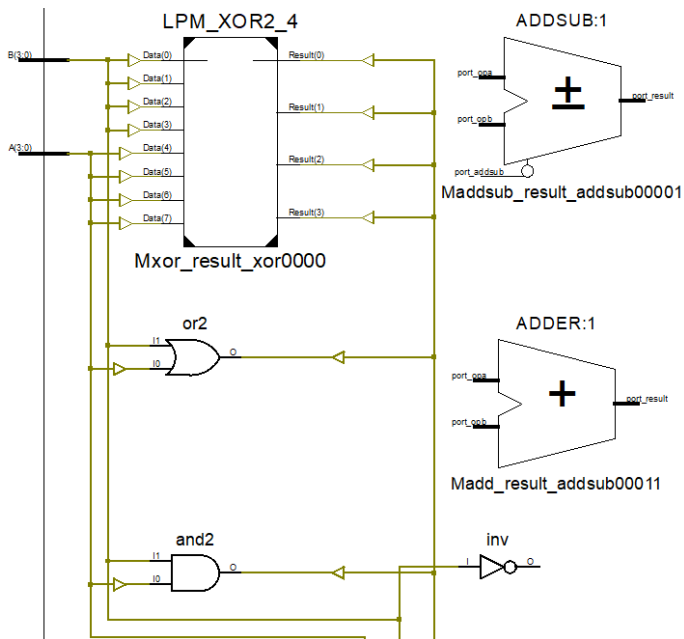 


Y(3:0)
CARRY_SIGN

 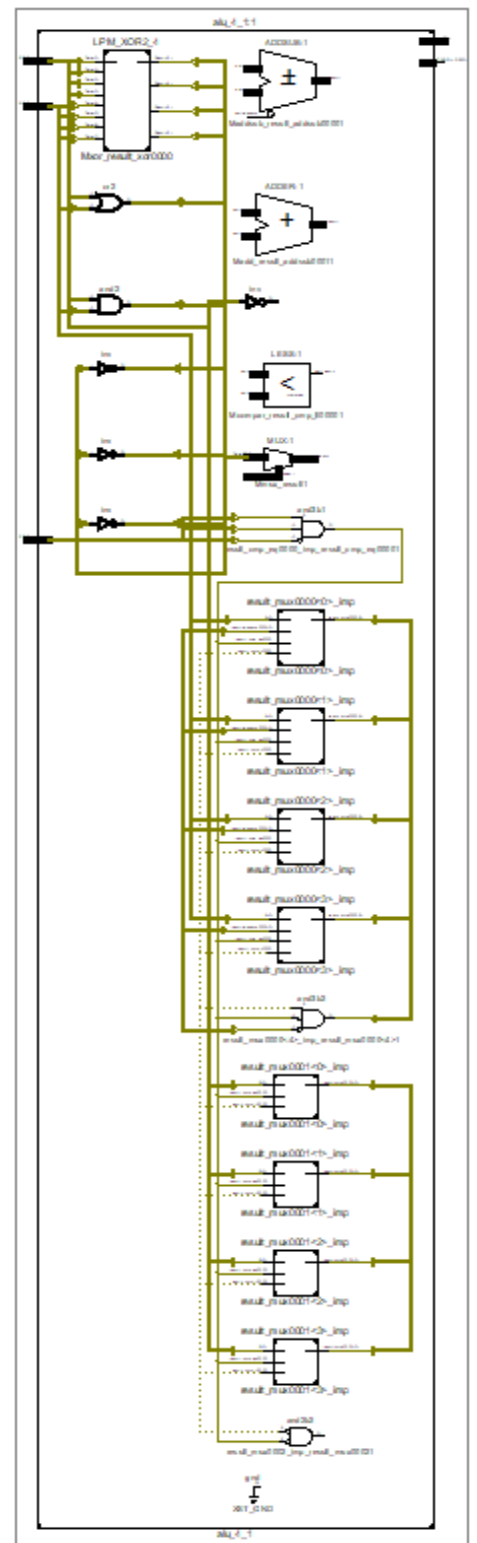

TECHNOLOGY SCHEMATIC

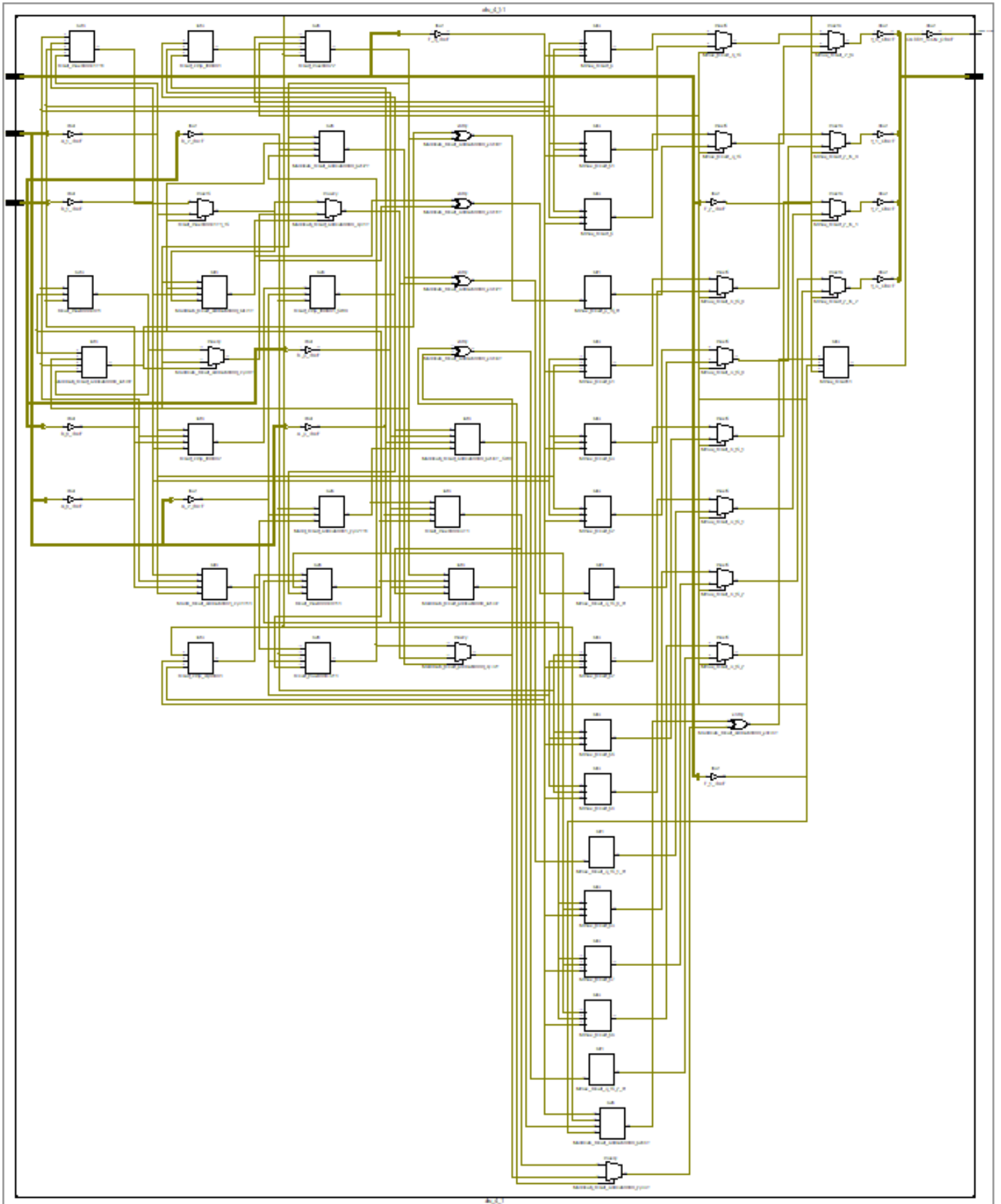

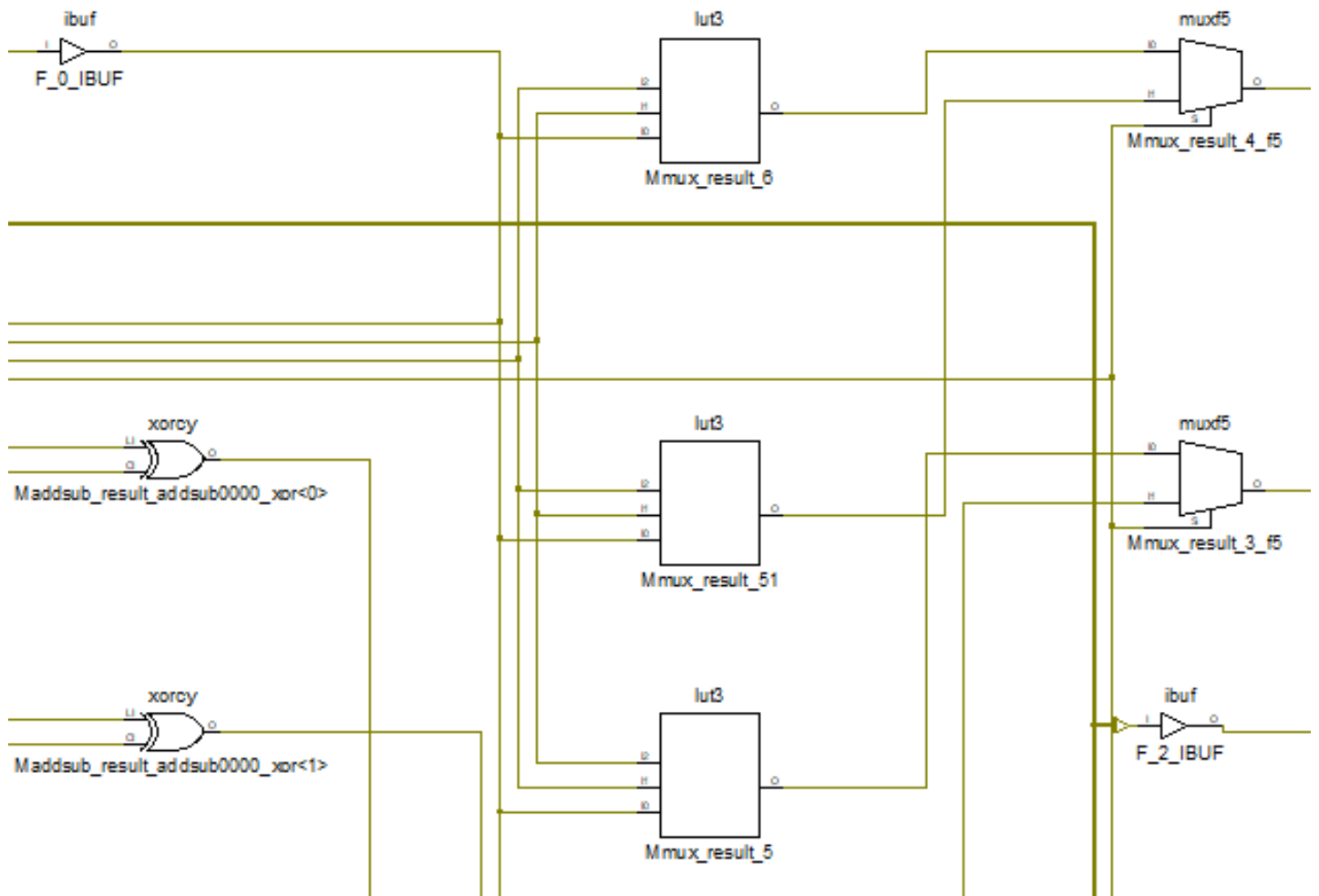

SYNTHESIS REPORT

1) Device Utilisation Summary

=====

* Final Report *

=====

Final Results

RTL Top Level Output File Name : alu_4_1.ngr
Top Level Output File Name : alu_4_1
Output Format : NGC
Optimization Goal : Speed
Keep Hierarchy : No

Design Statistics

IOs : 16

Cell Usage :

BELS : 57
LUT1 : 4
LUT3 : 18
LUT4 : 13
MUXCY : 4
MUXF5 : 9
MUXF6 : 4
XORCY : 5
IO Buffers : 16
IBUF : 11
OBUF : 5

=====

Device utilization summary:

Selected Device : 3s250epq208-5

Number of Slices: 19 out of 2448 0%
Number of 4 input LUTs: 35 out of 4896 0%
Number of IOs: 16
Number of bonded IOBs: 16 out of 158 10%

Partition Resource Summary:

No Partitions were found in this design.

2) TIMING REPORT

NOTE: THESE TIMING NUMBERS ARE ONLY A SYNTHESIS ESTIMATE.

FOR ACCURATE TIMING INFORMATION PLEASE REFER TO THE TRACE REPORT
GENERATED AFTER PLACE-and-ROUTE.

Clock Information:

No clock signals found in this design

Asynchronous Control Signals Information:

No asynchronous control signals found in this design

Timing Summary:

Speed Grade: -5

Minimum period: No path found

Minimum input arrival time before clock: No path found

Maximum output required time after clock: No path found

Maximum combinational path delay: 13.714ns

Timing Detail:

All values displayed in nanoseconds (ns)

TESTBENCH PROGRAM

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

ENTITY alu_4_1_tb IS
END alu_4_1_tb;

ARCHITECTURE behavior OF alu_4_1_tb IS

    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT alu_4_1
    PORT(
        A : IN  std_logic_vector(3 downto 0);
        B : IN  std_logic_vector(3 downto 0);
        F : IN  std_logic_vector(2 downto 0);
        Y : OUT std_logic_vector(3 downto 0);
        CARRY_SIGN : OUT std_logic
    );
    END COMPONENT;

    --Inputs
    signal A : std_logic_vector(3 downto 0) := "1010";
    signal B : std_logic_vector(3 downto 0) := "1100";
    signal F : std_logic_vector(2 downto 0) := (others => '0');

    --Outputs
    signal Y : std_logic_vector(3 downto 0);
    signal CARRY_SIGN : std_logic;
    -- No clocks detected in port list. Replace <clock> below with
    -- appropriate port name


BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: alu_4_1 PORT MAP (
        A => A,
        B => B,
        F => F,
        Y => Y,
        CARRY_SIGN => CARRY_SIGN
    );

    -- Clock process definitions

    -- Stimulus process
    stim_proc: process
    begin
        F <= F+1;
        WAIT FOR 40 ns;
    end process;
END;
```

ISIM WAVEFORMS

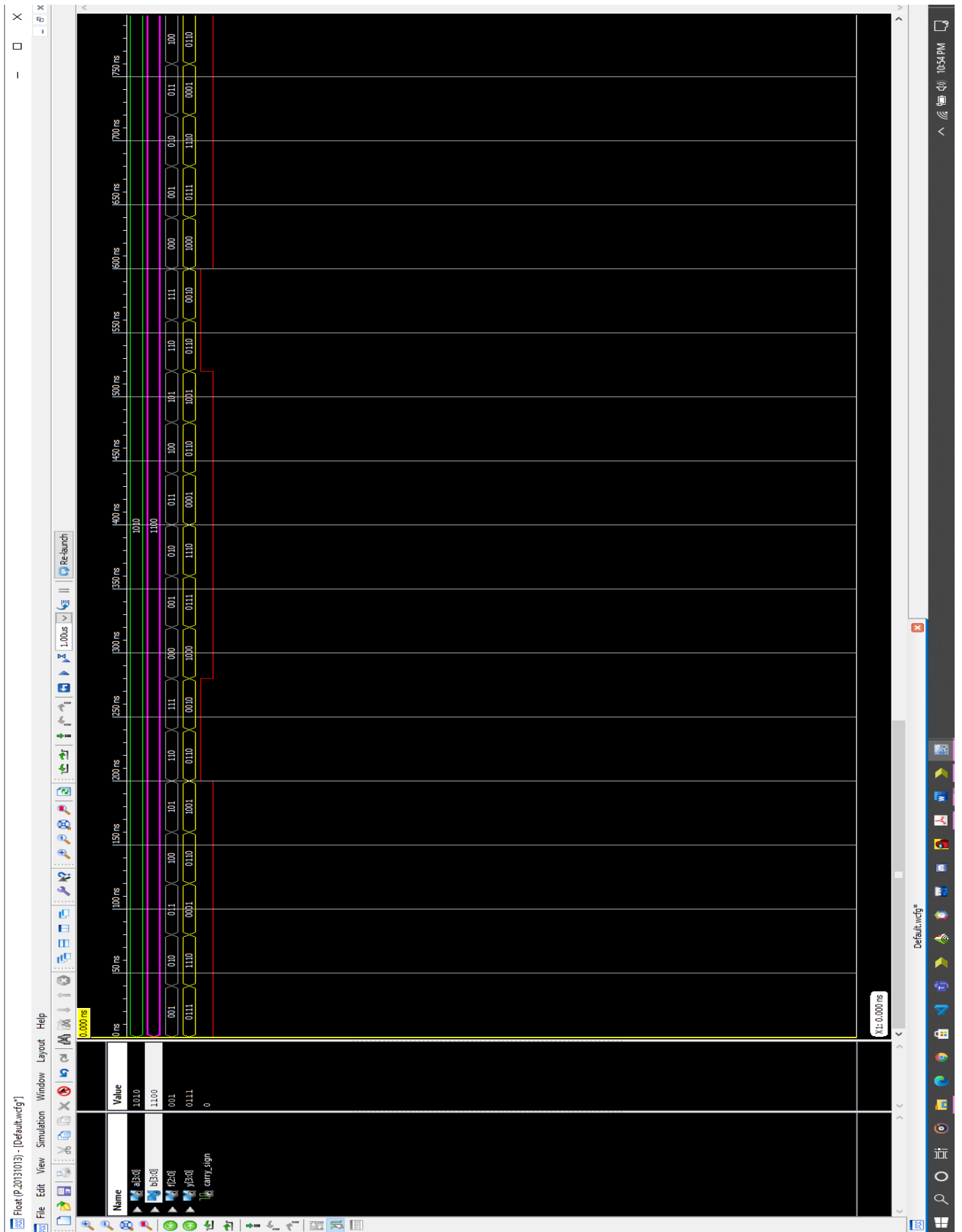

PIN-LOCKING REPORT

PlanAhead Generated physical constraints

NET "A[3]" LOC = P205;

NET "A[2]" LOC = P206;

NET "A[1]" LOC = P203;

NET "A[0]" LOC = P200;

NET "B[3]" LOC = P192;

NET "B[2]" LOC = P193;

NET "B[1]" LOC = P189;

NET "B[0]" LOC = P190;

NET "F[2]" LOC = P179;

NET "F[1]" LOC = P180;

NET "F[0]" LOC = P177;

NET "Y[3]" LOC = P165;

NET "Y[2]" LOC = P167;

NET "Y[1]" LOC = P163;

NET "Y[0]" LOC = P164;

Conclusion:

Thus we have :

- 1) Modeled a 4-bit ALU using Behavioral Modeling Style.
- 2) Observed following Schematics: **RTL & Technology Schematics** generated **Post-Synthesis**.
- 3) Interpreted **Device Utilization Summary** in terms of LUTs, SLICES, IOBs, Multiplexers & D FFs used out of the available device resources.
- 4) Interpreted the TIMING Report in terms of Maximum combinational delay as indicative of the Maximum Operating Frequency.
- 5) Written a TESTBENCH to verify the functionality of 4-bit ALU & verified the functionality as per the TRUTH-TABLE by observing ISIM Waveforms.
- 6) Used PlanAhead Editor for pin-locking.
- 7) Prototyped the FPGA **XC3S250EPQ208-5** to realize 4-bit ALU & verified its operation by giving suitable input combinations.