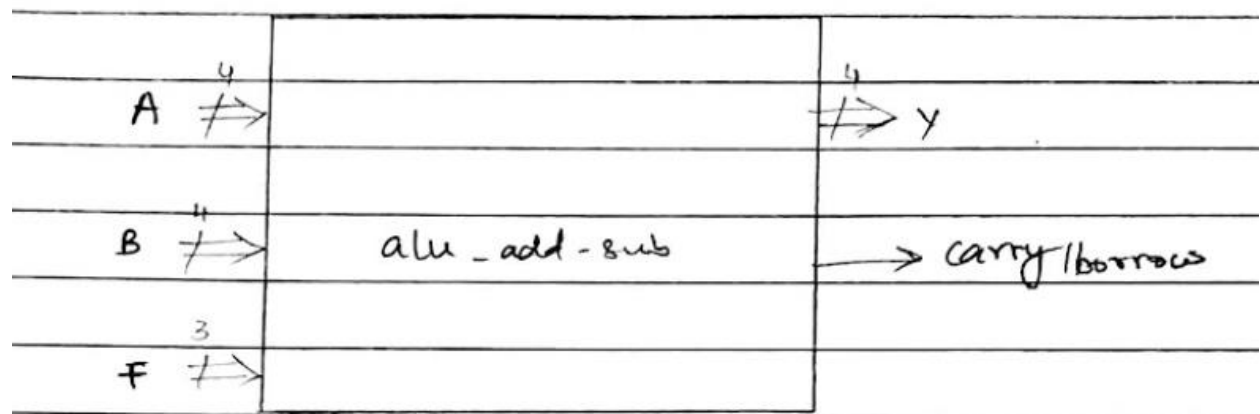


TITLE PAGE

Class	:	BE-08
Roll No.	:	42410
Assignment No.	:	01
Assignment Name	:	4 -bit ALU (Arithmetic Logic Unit)
Date of Performance	:	

Block Diagram:



A, B : 4 bit operands

F : 3 bit function bus

Y : 4 bit sum / difference logic o/p

carry - borrow : carry or borrow

Truth Table:

function Bus			operations
F(2)	F(1)	F(0)	
0	0	0	$A \cdot B$
0	0	1	$\overline{A} \cdot B$
0	1	0	$A + B$
0	1	1	$\overline{A + B}$
1	0	0	$A \oplus B$
1	0	1	$\overline{A \oplus B}$
1	1	0	$A \text{ add } B$
1	1	1	$A - B$

MAIN VHDL PROGRAM



```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_unsigned.ALL;
use IEEE.NUMERIC_STD.ALL;



entity alu_add_sub is
  Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
        B : in STD_LOGIC_VECTOR (3 downto 0);
        F : in STD_LOGIC_VECTOR (2 downto 0);
        Carry_borrow : out STD_LOGIC;
        Y : out STD_LOGIC_VECTOR (3 downto 0));
end alu_add_sub;

architecture alu_add_sub_arch of alu_add_sub is
  signal result: std_logic_vector(4 downto 0):="00000";
begin
  PROCESS(A,B,F)
  BEGIN
    CASE F IS
      WHEN "000" =>
        result <= '0' & (A AND B);
      WHEN "001" =>
        result <= '0' & (A NAND B);
      WHEN "010" =>
        result <= '0' & (A OR B);
      WHEN "011" =>
        result <= '0' & (A NOR B);
      WHEN "100" =>
        result <= '0' & (A XOR B);
      WHEN "101" =>
        result <= '0' & (A XNOR B);
      WHEN "110" =>
        result <= ('0' & A) + ('0' & B);
      WHEN OTHERS =>
        if a < b then
          result <= not(('0' & A) + ('0' & not(B)+1))+1;
        else
          result <= ('0' & A) - ('0' & B);
        end if;
    END CASE;
  END PROCESS;


  Y <= result(3 downto 0);
  Carry_borrow <= result(4);
end alu_add_sub_arch;
```



RTL SCHEMATIC

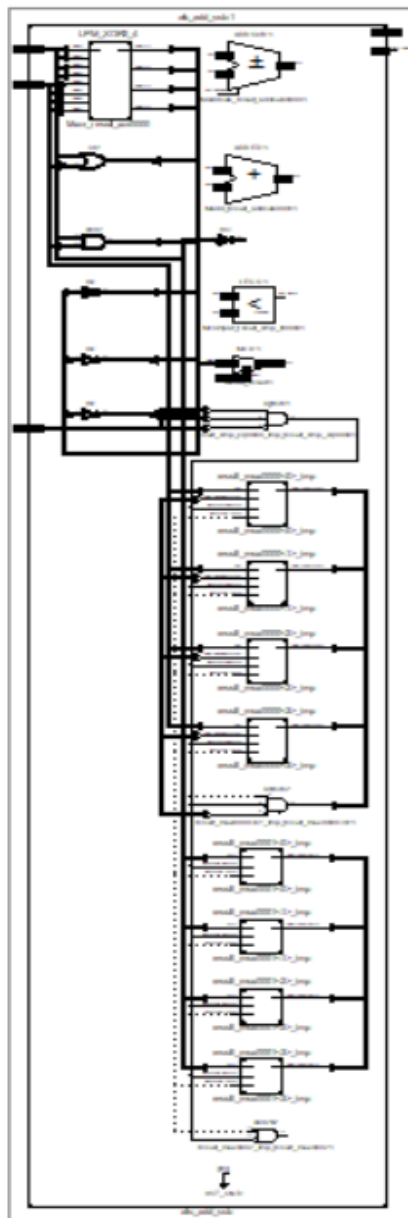 

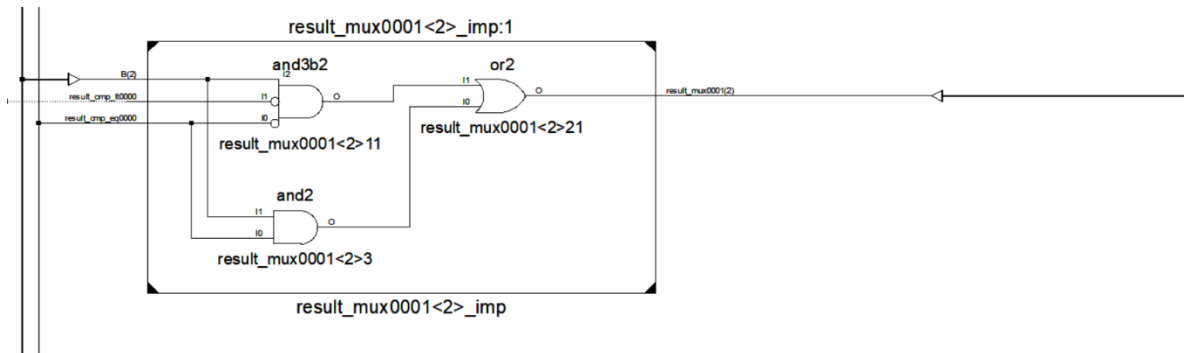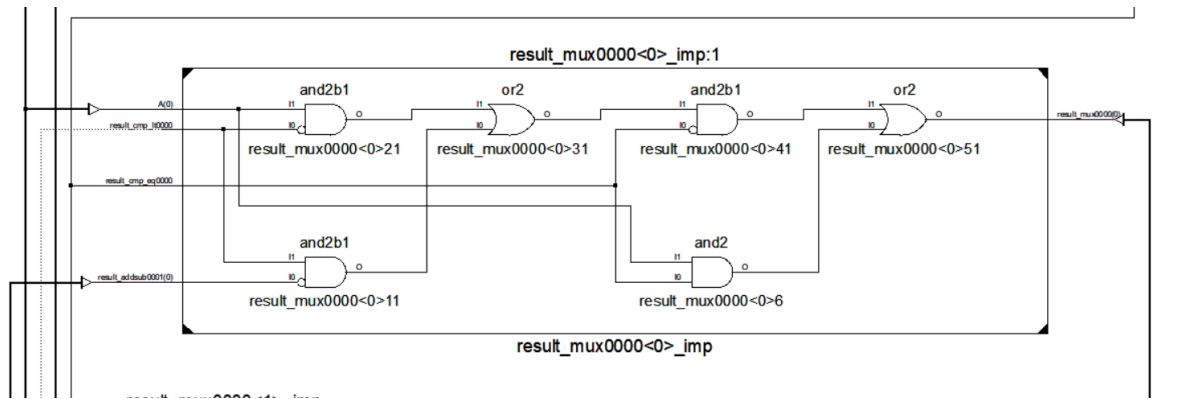

TECHNOLOGY SCHEMATIC

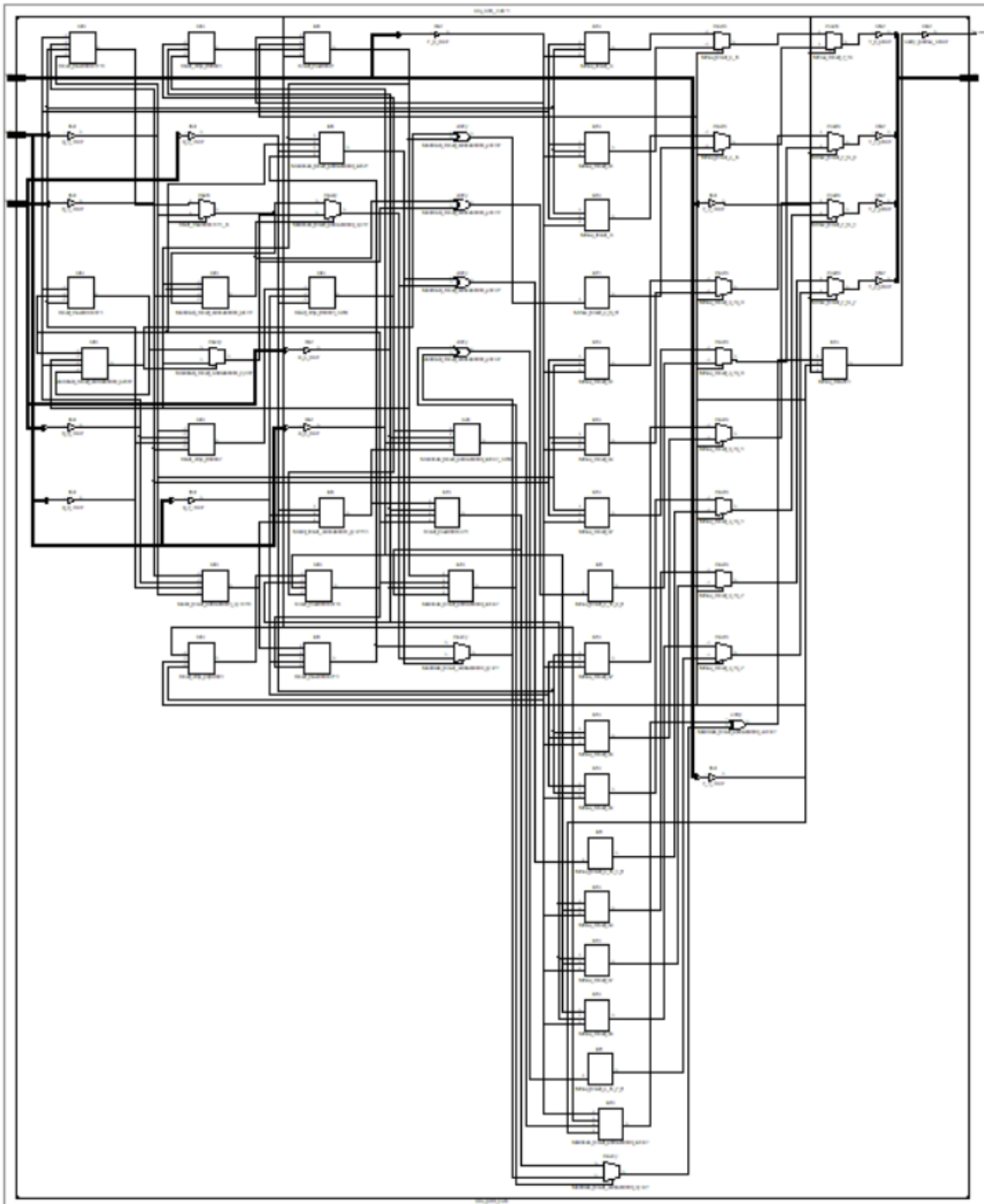

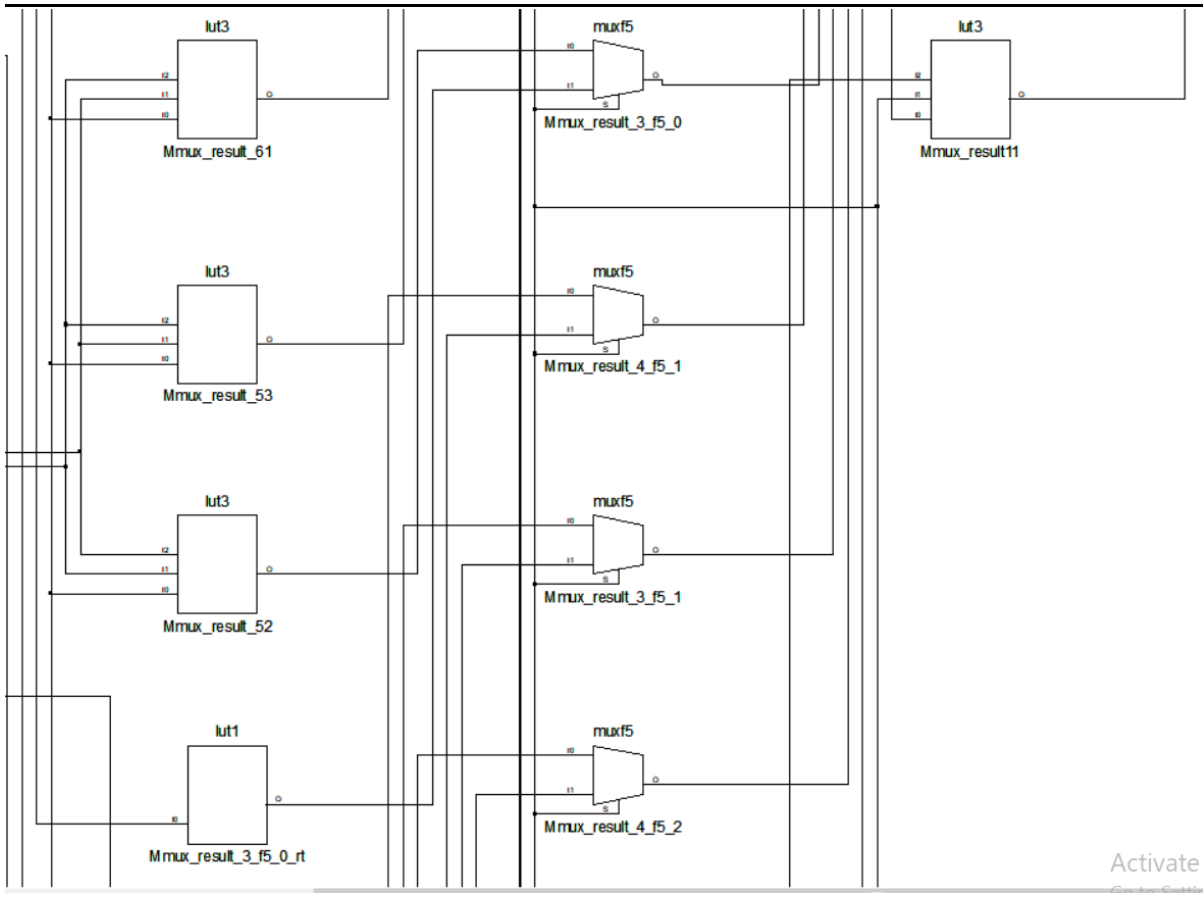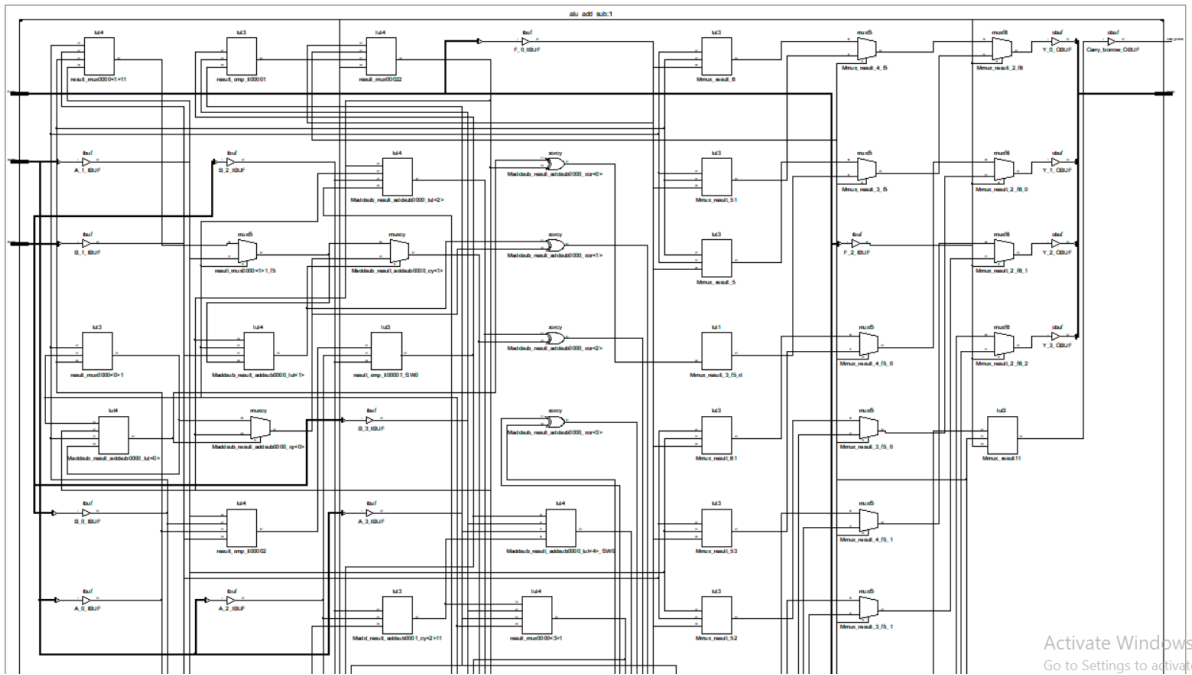

Activate Windows
Go to Settings to activate

Activate Windows
Go to Settings to activate

SYNTHESIS REPORT

a) Device Utilisation Summary

```
=====
*                      Final Report                      *
=====

Final Results
RTL Top Level Output File Name  : alu_add_sub.ngc
Top Level Output File Name     : alu_add_sub
Output Format                   : NGC
Optimization Goal               : Speed
Keep Hierarchy                  : No

Design Statistics
# IOs                          : 16

Cell Usage :
# BELS                      : 57
# LUT1                      : 4
# LUT3                      : 18
# LUT4                      : 13
# MUXCY                     : 4
# MUXF5                     : 9
# MUXF6                     : 4
# XORCY                     : 5
# IO Buffers                : 16
# IBUF                      : 11
# OBUF                      : 5
=====
```

Device utilization summary:

Selected Device : 3s250epq208-5

Number of Slices:	19 out of 2448	0%
Number of 4 input LUTs:	35 out of 4896	0%
Number of IOs:	16	
Number of bonded IOBs:	16 out of 158	10%

Partition Resource Summary:

No Partitions were found in this design.

b) Timing Report

=====

TIMING REPORT

NOTE: THESE TIMING NUMBERS ARE ONLY A SYNTHESIS ESTIMATE.
FOR ACCURATE TIMING INFORMATION PLEASE REFER TO THE TRACE REPORT
GENERATED AFTER PLACE-and-ROUTE.

Clock Information:

No clock signals found in this design

Asynchronous Control Signals Information:

No asynchronous control signals found in this design

Timing Summary:

Speed Grade: -5

Minimum period: No path found

Minimum input arrival time before clock: No path found

Maximum output required time after clock: No path found

Maximum combinational path delay: 13.714ns

Timing Detail:

All values displayed in nanoseconds (ns)

TESTBENCH PROGRAM

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
use ieee.std_logic_unsigned.all;

ENTITY alu_add_sub_tb IS
END alu_add_sub_tb;

ARCHITECTURE alu_add_sub_arch OF alu_add_sub_tb IS

-- Component Declaration for the Unit Under Test (UUT)

    COMPONENT alu_add_sub
        PORT(
            A : IN  std_logic_vector(3 downto 0);
            B : IN  std_logic_vector(3 downto 0);
            F : IN  std_logic_vector(2 downto 0);
            Carry_borrow : OUT std_logic;
            Y : OUT std_logic_vector(3 downto 0)
        );
    END COMPONENT;

    --Inputs
    signal A : std_logic_vector(3 downto 0) := "1000";
    signal B : std_logic_vector(3 downto 0) := "1001";
    signal F : std_logic_vector(2 downto 0) := (others => '0');

    --Outputs
    signal Carry_borrow : std_logic;
    signal Y : std_logic_vector(3 downto 0);
-- No clocks detected in port list. Replace <clock> below with
-- appropriate port name
    BEGIN
        -- Instantiate the Unit Under Test (UUT)
        uut: alu_add_sub PORT MAP (
            A => A,
            B => B,
            F => F,
            Carry_borrow => Carry_borrow,
            Y => Y
        );
        stim_proc: process
        begin
            F <= F+1;
            wait for 40 ns;
        end process;

    END;
```

ISIM WAVEFORMS



UCF FILE

PlanAhead Generated physical constraints

```
NET "A[3]" LOC = P205;
NET "A[2]" LOC = P206;
NET "A[1]" LOC = P203;
NET "A[0]" LOC = P200;
NET "B[3]" LOC = P192;
NET "B[2]" LOC = P193;
NET "B[1]" LOC = P189;
NET "B[0]" LOC = P190;
NET "F[2]" LOC = P179;
NET "F[1]" LOC = P180;
NET "F[0]" LOC = P177;
NET "Y[3]" LOC = P165;
NET "Y[2]" LOC = P167;
NET "Y[1]" LOC = P163;
NET "Y[0]" LOC = P164;
```

CONCLUSION:

Thus, we have:

- 1) Modelled 4-Bit ALU Interfacing using Behavioural Modelling Style.
- 2) Observed following Schematics: **RTL & Technology Schematics** generated **Post-Synthesis**.
- 3) Interpreted **Device Utilisation Summary** in terms of LUTs , SLICES , IOBs , Multiplexers & D FFs used out of the available device resources.
- 4) Interpreted the TIMING Report in terms of Maximum combinational delay as indicative of the Maximum Operating Frequency.
- 5) Written a TESTBENCH to verify the functionality of 4-Bit ALU Interfacing & verified the functionality as per the TRUTH-TABLE, by observing ISIM Waveforms.
- 6) Used PlanAhead Editor for pin-locking.
- 7) Prototyped the FPGA **XC3S250EPQ208-5** to realize 4-Bit ALU Interfacing & verified its operation by giving suitable input combinations.