



Class	:	BE - 8
Roll. No	:	42410
Assignment No.	:	1.f
Assignment Name	:	Half Adder
Date of Performance	:	21-11-2020

⊕ (L.f) Half Adder :- Also Includes Assignment 2

$F = 90 \text{ nm}$

+ Symbol:-

Gate-level Schematic

 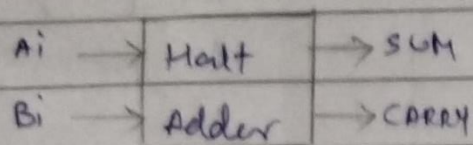

⊗ $SUM = A_i \oplus B_i$

$CARRY = A_i \cdot B_i$

TRUTH TABLE

A_i	B_i	SUM	CARRY
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

⊕ Approach $TQ \rightarrow MUX \rightarrow \text{LOGIC GATE}$



①

②


⊛ Assignment: I.F (continued...)

MUX-1 (EX-OR GATE)

MUX-2 (AND GATE)

 
 


⊛ COMBINED SCHEMATIC

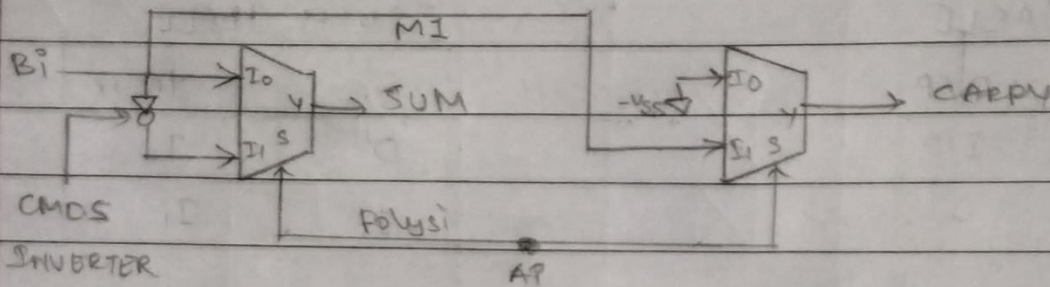

BLOCK DIAGRAM

⊛ COMBINED SCHEMATIC

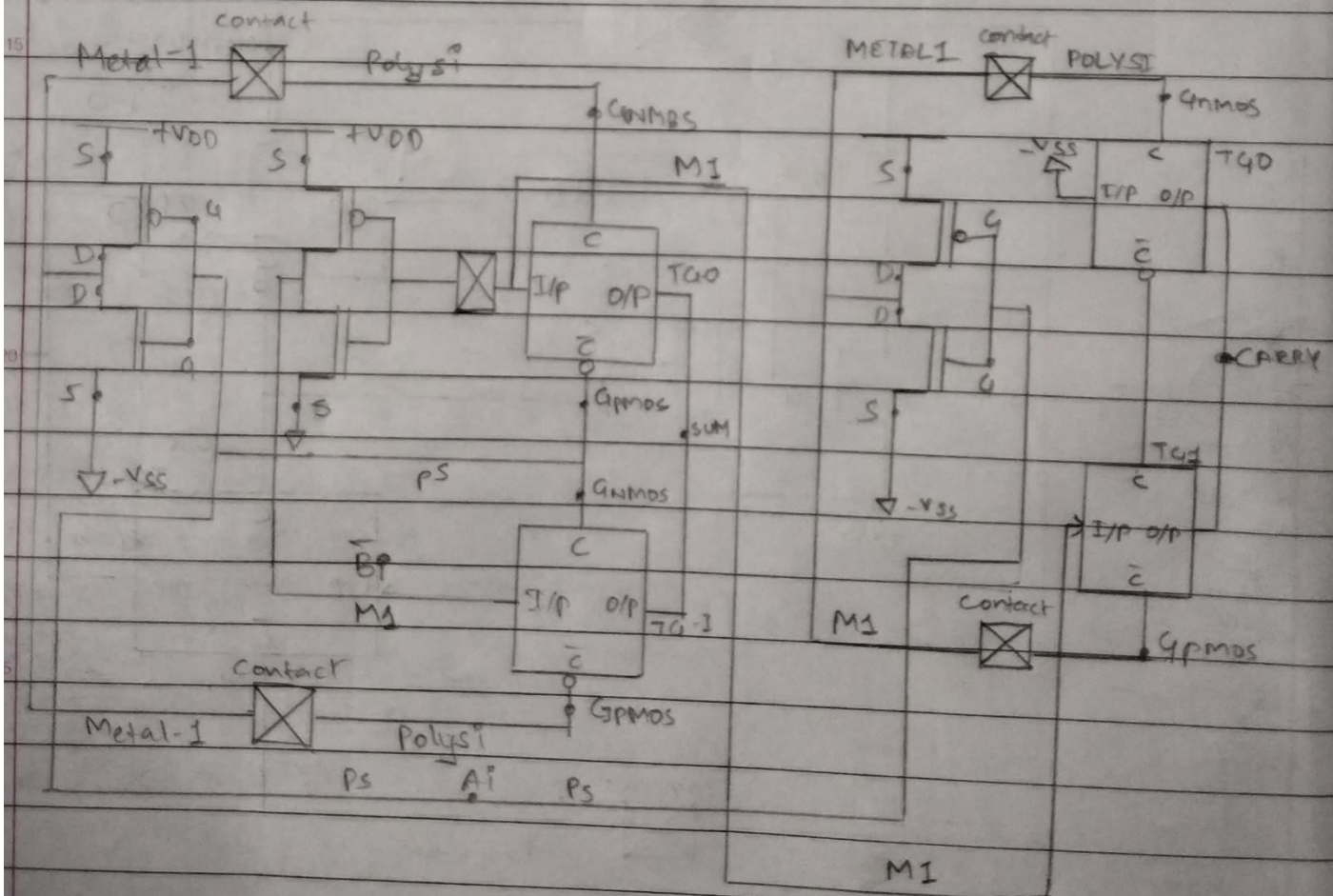 


LAYOUT

File View Edit Simulate Compile Analysis Help



5 lambda.
0.250um

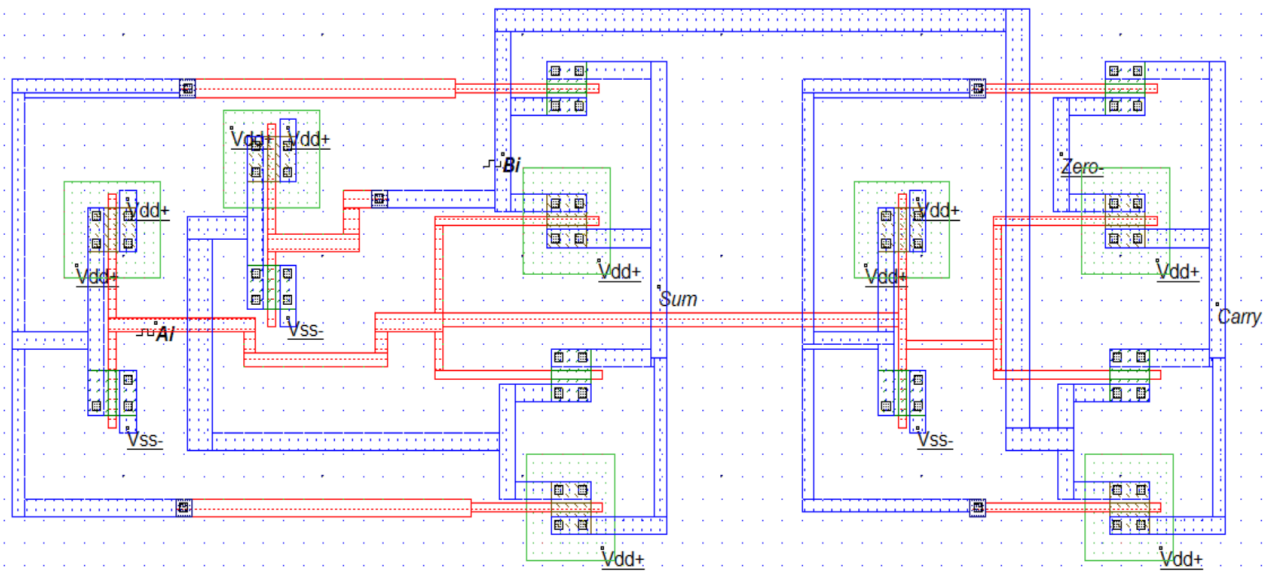


Saved 208 boxes in "F:\PART-B\Microwind 3.1 Full\rules\HALF_ADDER.MSK"

Bi


CMOS 90nm, 6 Metal Copper - strained SiGe - LowK (1.20V,2.50V)

WAVEFORMS

1. V vs T Waveform

 

V out, I out Waveform

 

Conclusions:

Thus, we have:

- 1) Drawn the LAYOUT for Half adder by using an EX-OR gate and an AND gate constructed by Multiplexers in 90 nm Foundry.
- 2) Simulated the LAYOUT to observe waveforms.
- 3) Verified its functionality as per TRUTH-TABLE.