

Class	:	BE - 8
Roll. No	:	42410
Assignment No.	:	B.1 (b, c)
Assignment Name	:	CMOS NAND and AND Gate
Date of Performance	:	12-11-2020


(*) (1.6) CMOS 2 i/p NAND Gate

(1.7) CMOS 2 i/p AND Gate

$F = 90\text{nm}$


SYMBOLS: —

2 i/p NAND GATE:

 

$$Y_{\text{NAND}} = \overline{A \cdot B}$$

2 i/p AND GATE:

 


$$Y_{\text{AND}} = A \cdot B$$

TRUTH TABLES

A	B	Y_{NAND}
0	0	1
0	1	1
1	0	1
1	1	0

A	B	Y_{AND}
0	0	0
0	1	0
1	0	0
1	1	1

Block Diagram

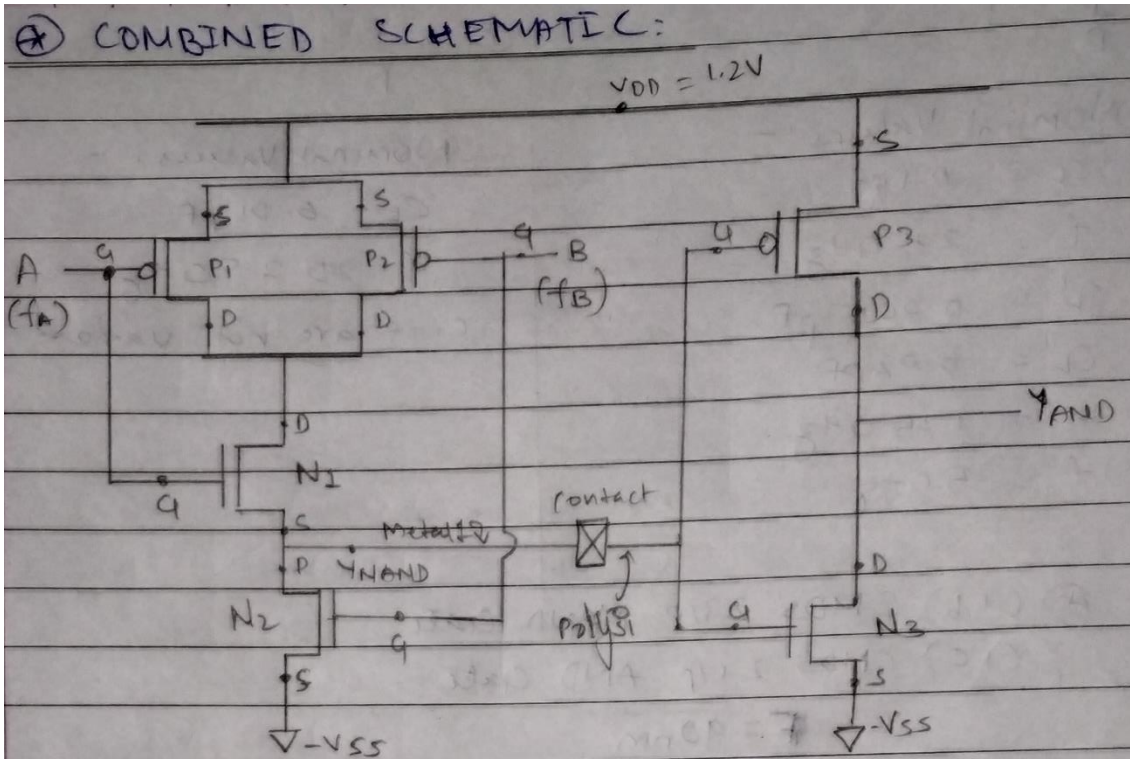

⊕ $f_B = 2 \times f_A$

⊕ Size of each PMOS Transistor (P1, P2, P3)

$$p = \left(\frac{500}{100} \right) \text{ nm} = 5$$

⊕ Size of each NMOS Transistor (N1, N2, N3)

$$n = \left(\frac{500}{100} \right) \text{ nm} = 5$$


⊕ Relative Size = $\frac{p}{n} = 1$

LAYOUT

File View Edit Simulate Compile Analysis Help



5 lambda
0.250µm

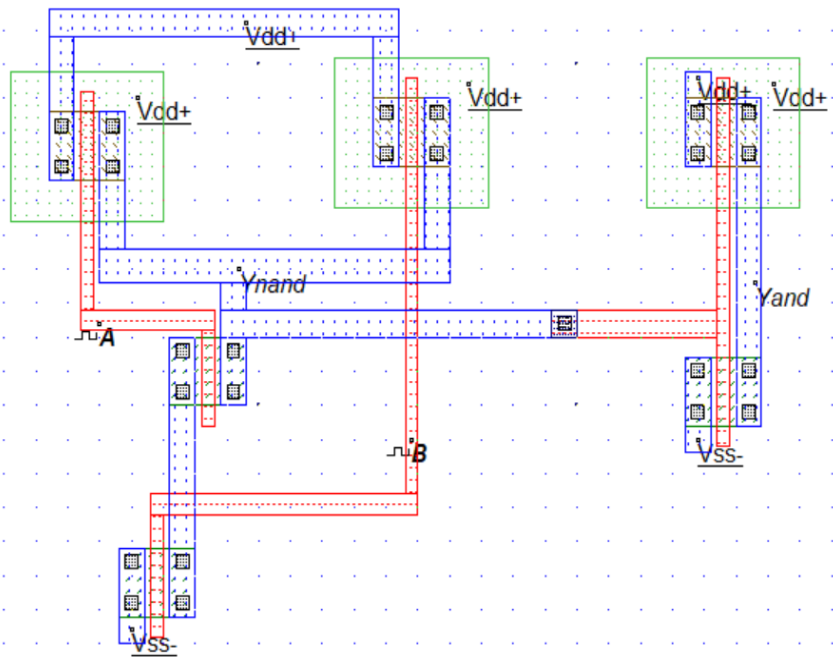


Saved 70 boxes in "F:\PART-B\Microwind 3.1 Full\rules\CMOS_NAND_42444.MSK"

Vdd

CMOS 90nm, 6 Metal Copper - strained SiGe - LowK (1.20V,2.50V)


WAVEFORMS

1. V vs T Waveform

 

SR.NO.	PARAMETER	VALUE
1)	$P_{dynamic}$	17.996 μW
2)	f_{max}	2.5 GHz

2. V out, I out Waveform

 

SR.NO.	PARAMETER	VALUE
1)	P_{dynamic}	17.660 μW
2)	f_{max}	2.5 GHz

Conclusions:

Thus, we have:

- 1) Drawn the LAYOUT for CMOS NAND and AND Gate using 90 nm Foundry.
- 2) Simulated the LAYOUT to observe waveforms.
- 3) Verified its functionality as per TRUTH-TABLE.
- 4) Noted the values of P_{dynamic} and f_{max} .